

EE6347 - Devices for AI and Neuromorphic Computing

Assignment 4

Task 1: Passive RRAM Array

- Create 3 x 3 RRAM Crossbar using the same model used in the Mid-Sem exam. (1 Mark)
- Follow the steps we followed in Tutorial 5. Use a V/3 scheme. Write the (0,0) cell and read currents through (1,0) and (2,2) (2 Marks = 1+1)
- Find the gap in (1,0) cell (1 Mark)

Task 2: 1T-1R RRAM Array

- Now create a 3 x 3 1T-1R Crossbar. You can use the same transistor settings we used in the Mid-Sem exam. (For writing, use a 1.2V pulse for 10ms to get an ON conductance of about 0.4nS) (1 Mark)
- Follow the same steps, but now instead of the V/3 scheme, just turn the WL of the 2nd and 3rd rows off. Use the BLs of the 1st row to program (0,0) appropriately (1 Mark)
- Now read the gap in (1,0) cell. Compare it with the previous part (2 Marks = 1+1)

Task 3: Row-by-Row writing

- Now instead of writing cell-by-cell. Write the following weights row-by-row. Report the number of pulse-cycles taken to program this. (1 Mark)

$$\begin{bmatrix} 1 & 0 & 1 \\ 0 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix}$$

- Find the gaps of all the cells and report them (3 Marks = 1+1+1)